



**Team Project**


Emmanuel Freduah-Agyemang, Valerie Maame Abena Ackon

CE 322: Digital System Design

24<sup>th</sup> July 2024

The purpose of this project was to create a digital system that serves as an electronic scoreboard for a lawn tennis court at Ashesi's sports complex.. Our team was tasked with designing the scoreboard to display scores in the traditional lawn tennis form which progresses from "Love/Lo"(0) to 15 then to 30 then finally 40.
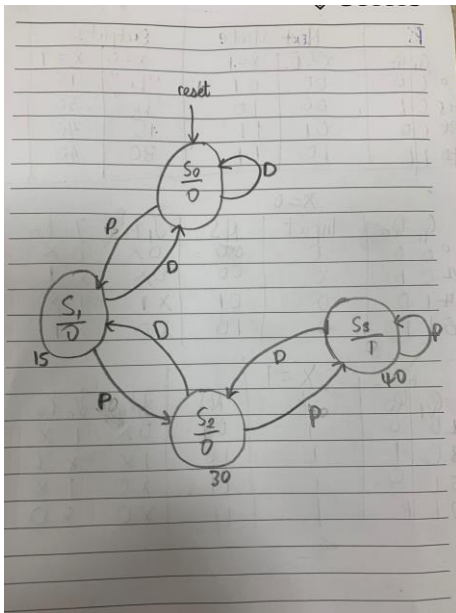
#### Moore machine of our counter and states



#### Our tables with our present state & next state

Commented [VA1]: Emmanuel Nhyira Freduah  
Agyemang proud of you and your spelling

PS		Next State		Outputs	
$Q_1 Q_0$		$X=0$	$X=1$	$X=0$	$X=1$
0 0		00	01	"L"	15
0 1		00	10	"L"	30
1 0		01	11	15	40
1 1		10	11	30	40

$X=0$		$X=1$	
$Q_1 Q_0$	Input	$N_1$	$J_1 K_1$
0 0	0	00	0X
0 1	0	00	0X
1 0	0	01	X1
1 1	0	10	X0

$Q_1 Q_0$	Input	$N_1$	$J_1 K_1$
0 0	1	00	0X
0 1	1	10	1X
1 0	1	11	X0
1 1	1	11	X0

#### Our kmaps and output table

$J_1$		$K_1$	
$Q_1 Q_0$		$Q_1 Q_0$	
0 0	0	0 0	0
0 1	0	0 1	0
1 0	1	1 0	1
1 1	1	1 1	1

$J_0$		$K_0$	
$Q_1 Q_0$		$Q_1 Q_0$	
0 0	0	0 0	0
0 1	0	0 1	0
1 0	1	1 0	1
1 1	1	1 1	1

$J_1$		$K_1$	
$Q_1 Q_0$		$Q_1 Q_0$	
0 0	0	0 0	0
0 1	0	0 1	0
1 0	1	1 0	1
1 1	1	1 1	1

$J_0$		$K_0$	
$Q_1 Q_0$		$Q_1 Q_0$	
0 0	0	0 0	0
0 1	0	0 1	0
1 0	1	1 0	1
1 1	1	1 1	1

$J_1$		$K_1$	
$Q_1 Q_0$		$Q_1 Q_0$	
0 0	0	0 0	0
0 1	0	0 1	0
1 0	1	1 0	1
1 1	1	1 1	1

$J_0$		$K_0$	
$Q_1 Q_0$		$Q_1 Q_0$	
0 0	0	0 0	0
0 1	0	0 1	0
1 0	1	1 0	1
1 1	1	1 1	1

We realised after building our Logisim circuit, that we designed for the system to count forward when  $D = 1$ , instead of when  $D = 0$ , as stated in the project document. Instead of going through

the entire design process again, we realised, that our equations corresponded with the actual operation of the circuit, and what we had to do was negate the D value. The equations below are the actual equations used in our implementation.

Renwriting?

$$Q_1$$

$$J = \overline{D} Q_0$$


$$K = D \overline{Q_0}$$
  

$$Q_2$$

$$J = Q_1 + \overline{D}$$

$$K = \overline{Q_1} + D$$

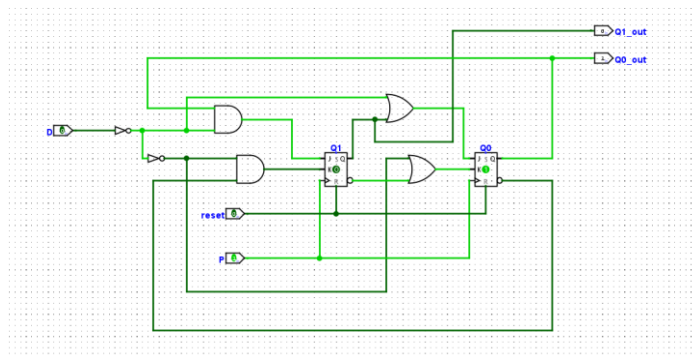Our circuit implemented with JK flipflops



Our final circuit with the seven segment displays

